

# ELEC2205 Electronic Design: D3 – Analogue Circuit Design Exercise

Jemma Watson

jw14g15

Tutor: Dr Tracy Melvin

## Abstract

Abstract!

## 1 Theoretical Design

The multi-stage amplifier circuit can be separated into two circuits; a common emitter stage followed by a common collector stage. Each stage can be analysed separately to calculate appropriate resistor and capacitor values before adding the circuits together.

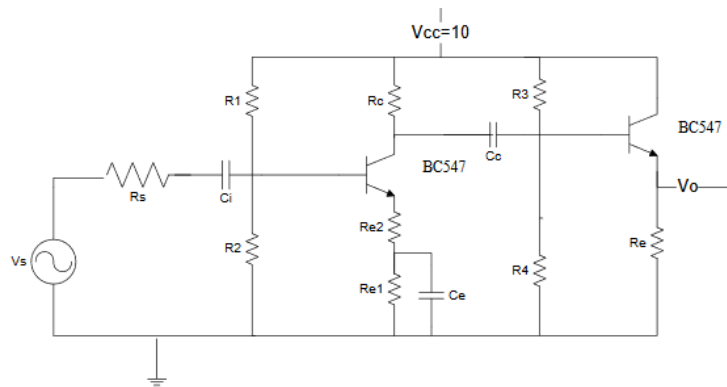


Figure 1: Two stage amplifier circuit

### 1.1 First stage: Common Emitter Circuit

The first circuit can be identified as a common emitter stage with partially by-passed emitter resistance.

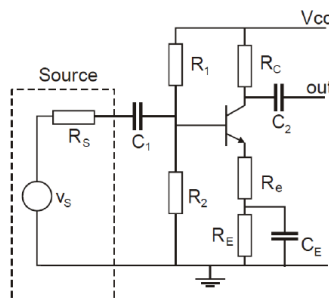


Figure 2: Common emitter stage

### 1.1.1 Mid-band Gain

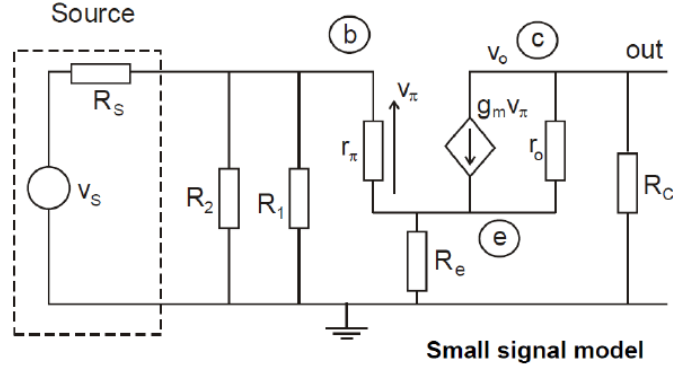


Figure 3: Small signal model of common emitter

By performing nodal analysis on Figure 3, the following equations can be obtained.

$$\begin{aligned} \text{Base: } \frac{v_b - v_s}{R_s} + \frac{v_b}{R_1} + \frac{v_b}{R_2} + \frac{v_b - v_e}{r_\pi} &= 0 \\ \frac{v_b - v_s}{R_s} + v_b \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{v_b - v_e}{r_\pi} &= 0 \end{aligned} \quad (1a)$$

$$\begin{aligned} \text{Emitter: } \frac{v_e - v_b}{r_\pi} + g_m v_\pi + \frac{v_e}{R_e} &= 0 \\ \frac{v_e - v_b}{r_\pi} - g_m(v_b - v_e) + \frac{v_e}{R_e} &= 0 \end{aligned} \quad (1b)$$

$$\text{Collector: } \frac{v_c}{R_c} + g_m(v_b - v_e) = 0 \quad (1c)$$

Rearranging equation 1b

$$\begin{aligned} v_e \left[ \frac{1}{r_\pi} + \frac{1}{R_e} + g_m \right] &= \frac{v_b}{r_\pi} + g_m v_b \\ v_e [R_e(1 + g_m r_\pi) + r_\pi] &= v_b R_e(1 + g_m r_\pi) \end{aligned}$$

Using the fact that  $g_m r_\pi = \beta$

$$v_e = v_b R_e \left( \frac{1 + \beta}{R_e(1 + \beta) + r_\pi} \right) \quad (2)$$

Modifying equation 1c as such

$$\begin{aligned} \frac{v_c}{R_c} + g_m(v_b - v_e) &= 0 \\ \frac{v_c}{R_c} + g_m v_b &= g_m v_e \\ v_e &= \frac{v_c}{g_m R_c} + v_b \end{aligned}$$

gives a value of  $v_e$  that can be substituted back into equation 2

$$\begin{aligned}
v_b R_e \left( \frac{1 + \beta}{R_e(1 + \beta) + r_\pi} \right) &= \frac{v_c}{g_m R_c} + v_b \\
v_b R_e(1 + \beta) &= \frac{v_c(R_e(1 + \beta) + r_\pi)}{g_m R_c} + v_b(R_e(1 + \beta) + r_\pi) \\
-v_b r_\pi &= \frac{v_c(R_e(1 + \beta) + r_\pi)}{g_m R_c} \\
\frac{v_c}{v_b} &= -\frac{r_\pi g_m R_c}{R_e(1 + \beta) + r_\pi} \\
\frac{v_c}{v_b} &= -\frac{\beta R_c}{R_e(1 + \beta) + r_\pi}
\end{aligned}$$

This may be approximated as

$$A = -\frac{\beta R_c}{R_e(1 + \beta) + r_\pi} \approx -\frac{R_c}{R_e} \quad (3)$$

### 1.1.2 Input Impedance

The impedance into the base terminal of the common emitter circuit is given by

$$\begin{aligned}
R_b &= \frac{v_b}{i_b} \\
\text{Where } i_b &= \frac{v_b - v_e}{r_\pi}
\end{aligned}$$

Therefore

$$\begin{aligned}
R_b &= \frac{v_b r_\pi}{v_b - v_e} \\
&= \frac{r_\pi}{1 - \frac{v_e}{v_b}}
\end{aligned} \quad (4)$$

From equation 2

$$\frac{v_e}{v_b} = R_e \left( \frac{1 + \beta}{R_e(1 + \beta) + r_\pi} \right) \quad (5)$$

Substituting equation 5 into 4 and rearranging gives

$$R_b = r_\pi + R_e(\beta + 1)$$

Therefore input impedance is the parallel combination of  $R_1$ ,  $R_2$  and  $R_b = r_\pi + R_e(\beta + 1)$

$$R_i = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_\pi + R_e(\beta + 1)} \right)^{-1} \quad (6)$$

### 1.1.3 Output Impedance

By examining 3 it can be seen that the output impedance will be

$$R_o = R_c \quad (7)$$

## 1.2 Common Collector Circuit

The second stage of the circuit consists of a straight forward common collector circuit as shown in figure 4.

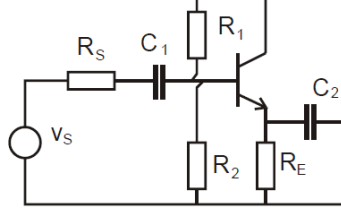


Figure 4: Common emitter stage

### 1.2.1 Mid-band Gain

To determine the mid-band gain, the circuit should be redrawn with respect to the small signal model, as in 5

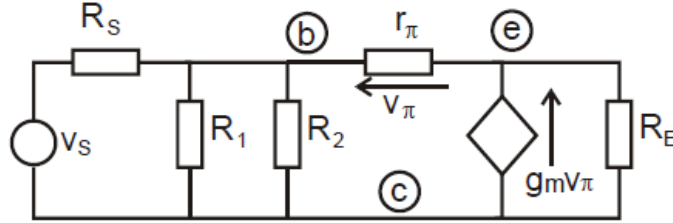


Figure 5: Common emitter stage

By using KVL on the emitter terminal we can establish that

$$\frac{v_e - v_s}{r_\pi} + g_m v_\pi + \frac{v_e}{R_E} = 0 \quad (8)$$

$$\frac{v_e - v_s}{r_\pi} + g_m (v_e - v_s) + \frac{v_e}{R_E} = 0$$

$$\frac{v_e - v_s}{r_\pi} + \frac{\beta(v_e - v_s)}{r_\pi} + \frac{v_e}{R_E} = 0$$

$$v_e(\beta R_E + R_E + r_\pi) = v_s R_E(\beta + 1)$$

$$\frac{v_e}{v_s} = \frac{R_E(\beta + 1)}{R_E(\beta + 1) + r_\pi} \quad (9)$$

Therefore gain  $\approx 1$

## 1.3 Input Impedance

Input impedance

$$R_i = \frac{v_s}{i_b} \quad (10)$$

Neglecting  $R_1, R_2$  and  $R_s$  gives

$$i_b = \frac{v_s - v_e}{r_\pi}$$

Substituting equation ?? into this gives

$$\begin{aligned} i_b &= \frac{v_s}{r_\pi} - \frac{v_s}{r_\pi} \left( \frac{R_E(\beta + 1)}{R_E(\beta + 1) + r_\pi} \right) \\ &= \frac{v_s}{r_\pi} \left( 1 - \frac{R_E(\beta + 1)}{R_E(\beta + 1) + r_\pi} \right) \\ &= \frac{v_s}{R_E(\beta + 1) + r_\pi} \end{aligned} \quad (11)$$

Therefore combining 10 and 11 gives

$$R_i = \frac{v_s}{i_b} = R_E(\beta + 1) + r_\pi \quad (12)$$

### 1.3.1 Output Impedance

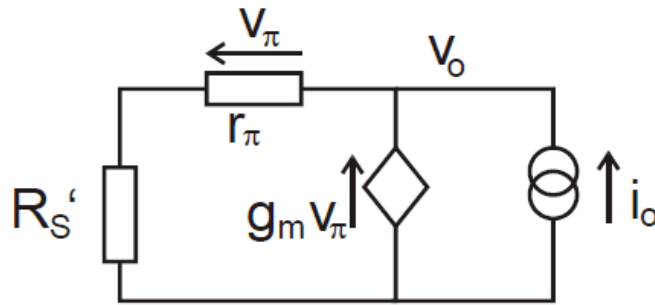


Figure 6: Common emitter stage

In figure 6 the Thevenin equivalent of the source resistances has been taken ( $R'_s$ )

$$R'_s = R_s || R_1 || R_2$$

By KVL

$$i_o + g_m v_\pi - \frac{v_o}{r_\pi R'_s} = 0 \quad (13)$$

$$v_\pi = -\frac{r_\pi v_o}{r_\pi + R'_s} \quad (14)$$

Substituting equation 13 into 14 gives

$$\begin{aligned} i_o - g_m \frac{r_\pi v_o}{r_\pi + R'_s} - \frac{v_o}{r_\pi R'_s} &= 0 \\ \frac{v_o(1 + g_m r_\pi)}{r_\pi + R'_s} &= i_b \\ R_o = \frac{v_o}{i_b} &= \frac{r_\pi + R'_s}{1 + \beta} \end{aligned} \quad (15)$$

This shows that the output impedance is dependant on the source and bias impedance.